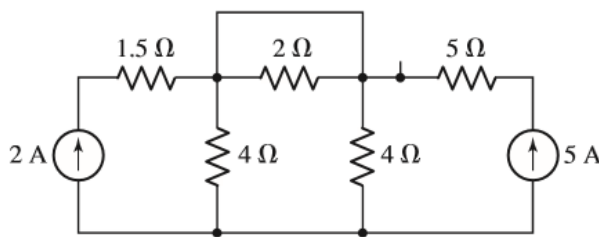


تاریخ تحویل: 20 مهر 1398

توجه: از همه سوالات کافیت 10 سوال را حل کنید، اما از هر دسته سوال (با شماره اصلی یکسان) نمی توانید بیش از یکی را

انتخاب کنید.

- 1- a. Plot the I-V characteristics of a $2\text{k}\Omega$, $1\text{M}\Omega$, and a 100Ω resistor on the same graph. Use a horizontal axis of 0 to 20 V and a vertical axis of 0 to 10 mA.
b. Comment on the steepness of the curve with decreasing levels of resistance.
c. Are the curves linear or nonlinear? Why?
- 2- Find the power, $p(t)$, supplied by the element shown in Figure below when $v(t) = 4\cos 3t$ V and $i(t) = \frac{\sin 3t}{12}$ A. Evaluate $p(t)$ at $t = 0.5$ and $t = 1$ s. observe that the power applied by this element has a positive value at some times and a negative value at other times.
(Answer: $p(0.5) = 0.0235$, $p(1) = -0.0466$)
- 3- Referring to the circuit depicted in Fig. 3.45, count the number of (a) nodes; (b) elements; (c) branches.



- 4-1. A CD player draws 125 mA when 4.5 V is applied. What is the internal resistance?
- 4-2. a. If an electric heater draws 9.5A when connected to a 120 V supply, what is the internal resistance of the heater?
b. Using the basic relationships, determine how much energy in joules (J) is converted if the heater is used for 2 h during the day.
- 4-3. The average plasma screen TV draws 339 W of power, whereas the average LCD TV draws 213 W. If each set was used 5 h/day for 365 days, what would be the cost savings for the LCD unit over the year if the cost is 11¢/kWh?

5-1. The current in a circuit element is:

$$i(t) = \begin{cases} 0 & t < 2 \\ 2 & 2 < t < 4 \\ -1 & 4 < t < 8 \\ 0 & 8 < t \end{cases}$$

where the units of current are A and the units of time are s. Determine the total charge that has entered a circuit element for $t \geq 0$.

5-2. The total charge $q(t)$, in coulombs, that enters the terminal of an electrode is:

$$q(t) = \begin{cases} 0 & t < 0 \\ 2t & 0 \leq t \leq 2 \\ 3 + e^{-2(t-2)} & t > 2 \end{cases}$$

Obtain the current passing that electrode.

6-1. The element currents and voltages shown in Figure P 1.7-3 are correct with one exception: the reference direction of exactly one of the element currents is reversed. Determine which reference direction has been reversed.

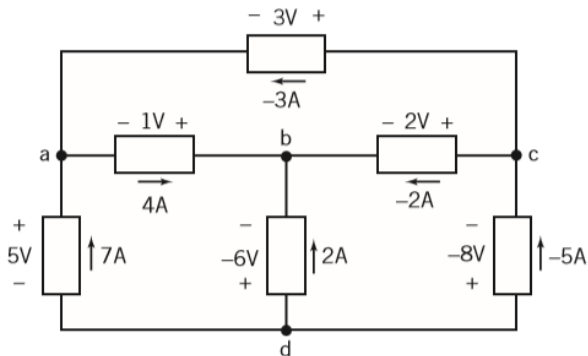


Figure P 1.7-3

6-2. Computer analysis of the circuit in Figure P 3.8-6 shows that $i_a = 0.5 \text{ mA}$ and $i_b = 4.5 \text{ mA}$. Was the computer analysis done correctly?


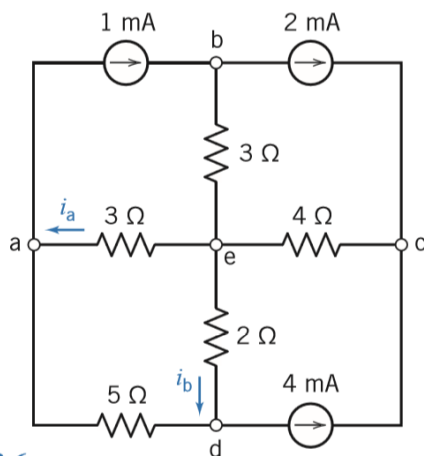



Figure P 3.8-6

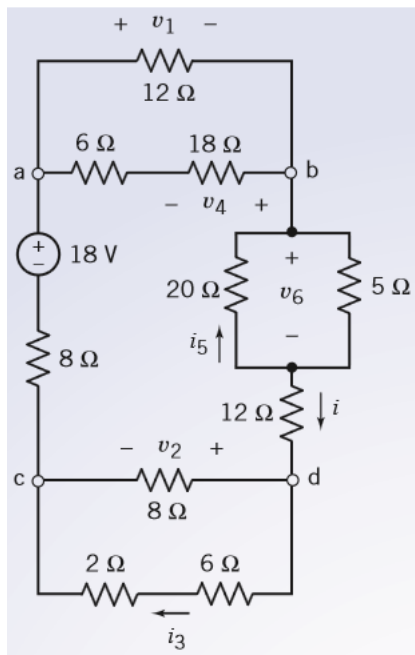1-7. با استفاده از مقاومت‌های سری و موازی و قانون تقسیم جریان و ولتاژ، ولتاژ و جریانهای مشخص شده در مدار زیر را به دست

آوردید. (جواب: $i_3 = 0.25 \text{ A}$, $v_4 = -3 \text{ V}$, $i_5 = -0.1 \text{ A}$, $v_6 = 2 \text{ V}$)




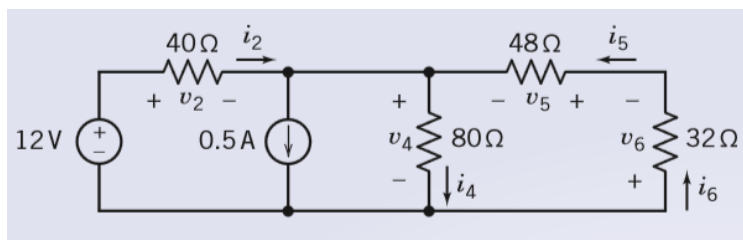7-2. Determine the values of the resistor voltages and currents for the circuit shown in Figure 3.7-1. (Answer: $i_4 = -0.05A$, $i_6 = 0.05A$, $v_2 = 16V$, $v_4 = -4V$, $v_5 = 2.4V$, $v_6 = 1.6V$)



7-3. (a) Determine a numerical value for each current and voltage (i_1 , v_1 , etc.) in the circuit of figure below.

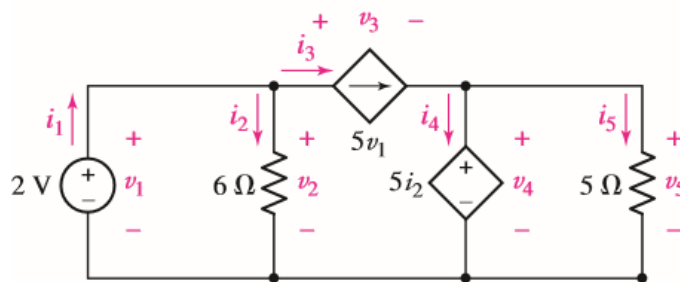(b) Calculate the power absorbed by each element and verify that they sum to zero



8-1. Determine the value of the voltage v_6 for the circuit shown in Figure P 3.2-20


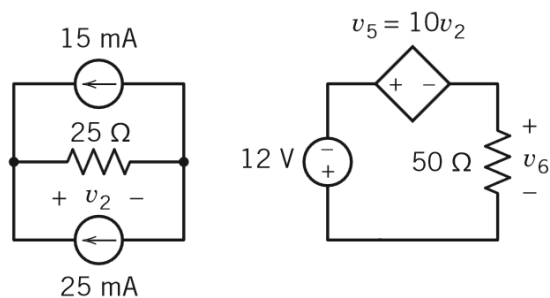



Figure P 3.2-20

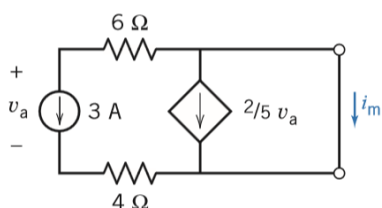8-2. Determine the value of the current i_m in Figure P 3.2-18a.




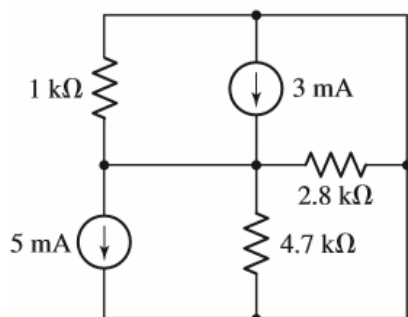8-3. Although drawn so that it may not appear obvious at first glance, the circuit of Fig. 3.73 is in fact a single-node-pair circuit.

- Determine the power absorbed by each resistor.
- Determine the power supplied by each current source.
- Show that the sum of the absorbed power calculated in (a) is equal to the sum of the supplied power calculated in (c).




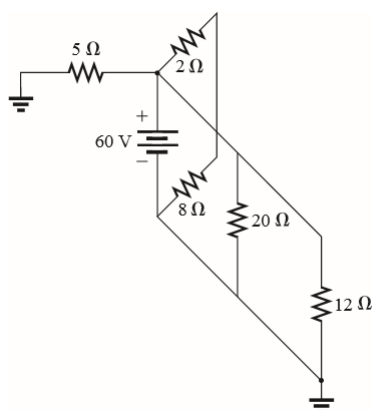8-4. Determine the power delivered by the dc battery in figure below.



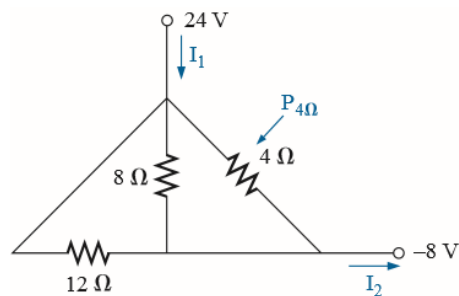8-5. For the network in figure below:

- Find the current I_1 .
- Calculate the power dissipated by the $4\ \Omega$ resistor.
- Find the current I_2 .



9-1. The voltage source in the circuit shown in Figure P 3.2-25 supplies $2W$ of power. The value of the voltage across the $25\text{-}\Omega$ resistor is $v_2 = 4V$. Determine the values of the resistance R_1 and of the gain G of the VCCS

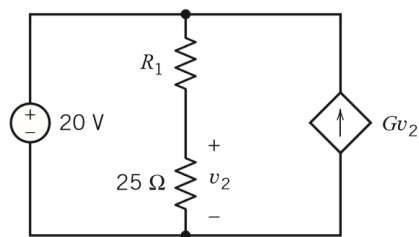


Figure P 3.2-25

9-2. Consider the circuit shown in Figure P 3.2-28. (a) Determine the value of the power supplied by each independent source. (b) Determine the value of the power received by each resistor. (c) Is power conserved?

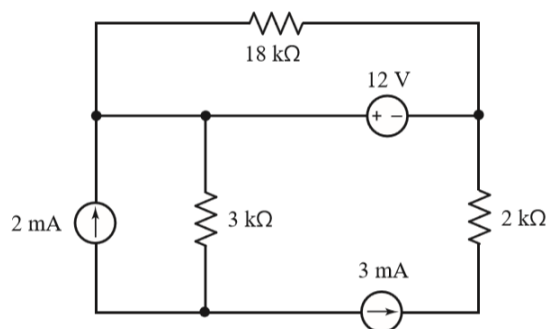


Figure P 3.2-28

9-3. Determine the power supplied by each source in the circuit shown in Figure P 3.5-2.



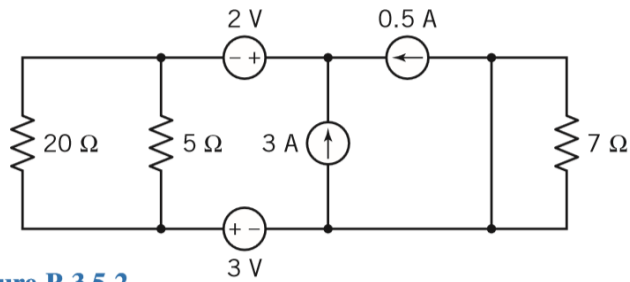


Figure P 3.5-2

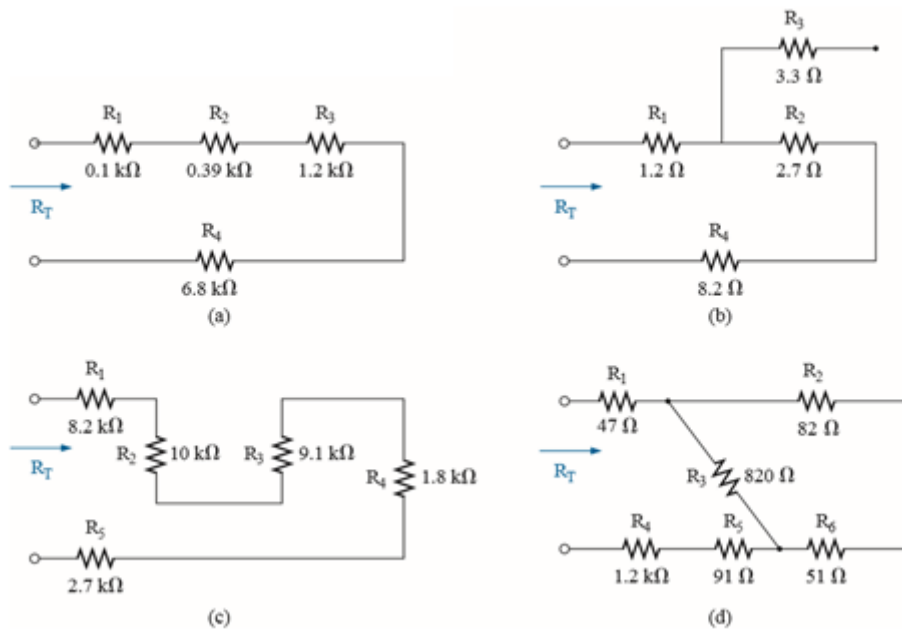
10-1. Find the total resistance R_T for each configuration in figure below. Note that only standard resistor values were used.



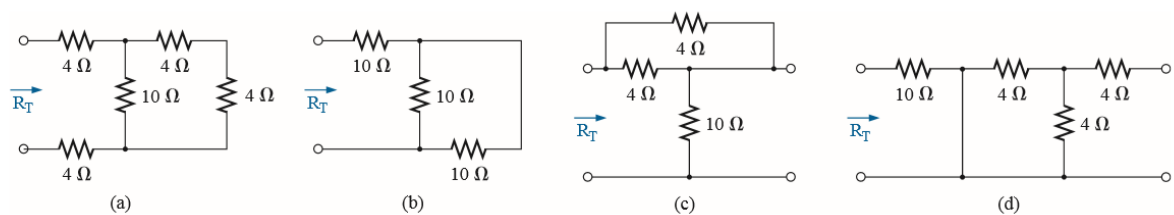10-2. Determine R_T for the networks in figure below:



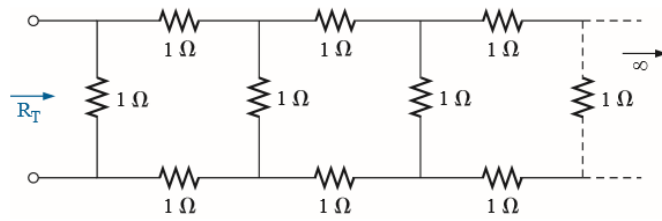10-3. Find the resistance for the network of figure below. **Hint! If it was infinite in length, how would the resistance looking into the next vertical 1Ω resistor compare to the desired resistance R_T ?**



10-4. Determine the value of the voltage v in Figure P3.4-8

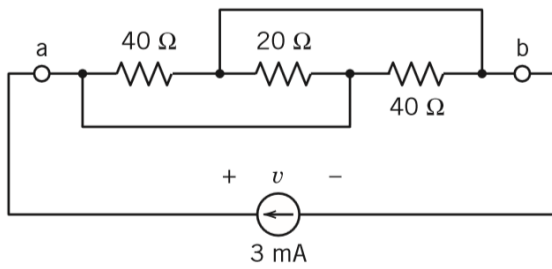


Figure P 3.4-8

10-5. The input to the circuit shown in Figure P 3.4-20 is the voltage source voltage V_s . The output is the voltage v_o . The output of this circuit is proportion to the input, that is $v_o = kV_s$. Determine the value of the constant of proportionality k .

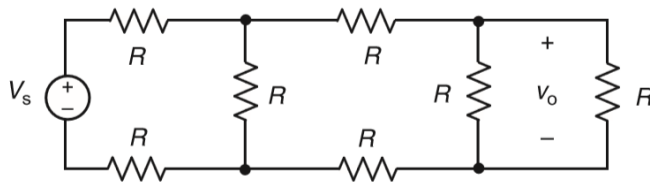


Figure P 3.4-20

10-6. All of the resistances in the circuit shown in Figure P 3.6-14 are multiples of R . Determine the value of R .


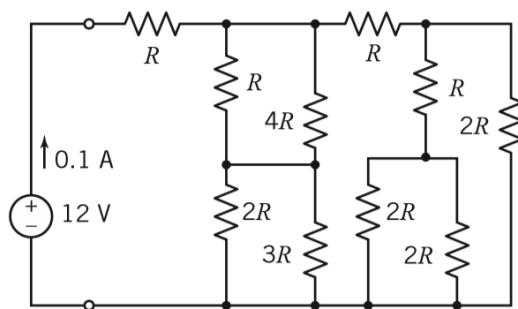


Figure P 3.6-14

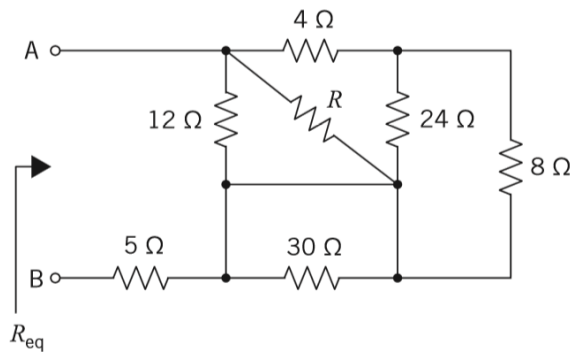10-7. Determine the value of the resistance R in the circuit shown in Figure P 3.6-21, given that $R_{eq} = 9\Omega$. (Answer: $R_{eq} = 15\Omega$)



- 10-8. Determine the value of the resistance R in the circuit shown in Figure P 3.6-22, given that $R_{eq} = 40\Omega$.



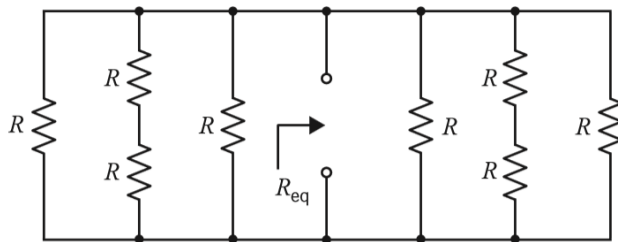


Figure P 3.6-22

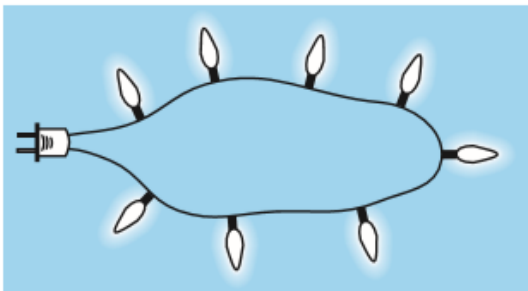
- 11-1. Eight holiday lights are connected in series as shown in figure below.
- If the set is connected to a 120 V source, what is the current through the bulbs if each bulb has an internal resistance of 8Ω ?
 - Determine the power delivered to each bulb.
 - Calculate the voltage drop across each bulb.
 - If one bulb burns out (that is, the filament opens), what is the effect on the remaining bulbs? Why?



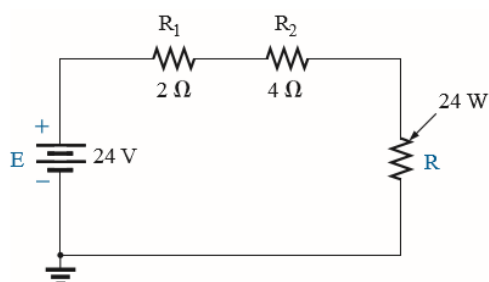- 11-2. For the conditions specified in figure below, determine the unknown resistance.



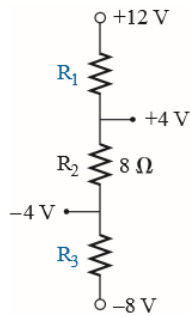11-3. Given the information appearing in figure below, find the level of resistance for R_1 and R_3 .



12-1. Determine the current i in the circuit shown in Figure P 3.4-4.


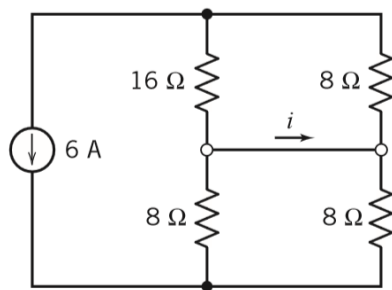


Figure P 3.4-4

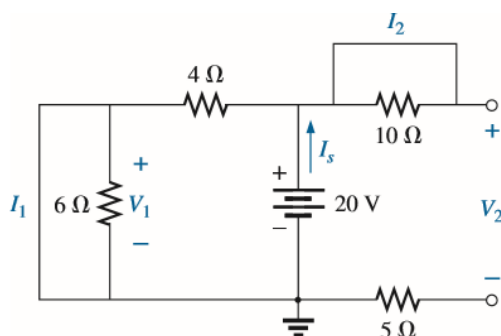12-2. For the network in below, determine:

- The short-circuit currents I_1 and I_2 .
- The voltages V_1 and V_2 .
- The source current I_s .



13-1. The circuit shown in Figure P 3.6-2a has been divided into three parts. In Figure P 3.6-2b, the rightmost part has been replaced with an equivalent circuit. The rest of the circuit has not been changed. The circuit is simplified further in Figure 3.6-2c. Now the middle and rightmost parts have been replaced by a single equivalent resistance. The leftmost part of the circuit is still unchanged.

(a) Determine the value of the resistance R_1 in Figure P 3.6-2b that makes the circuit in Figure P 3.6-2b equivalent to the circuit in Figure P 3.6-2a.

(b) Determine the value of the resistance R_2 in Figure P 3.6-2c that makes the circuit in Figure P 3.6-2c equivalent to the circuit in Figure P 3.6-2b.




(c) Find the current i_1 and the voltage v_1 shown in Figure P3.6-2c. Because of the equivalence, the current i_1 and the voltage v_1 shown in Figure P3.6-2b are equal to current i_1 and the voltage v_1 shown in Figure P 3.6-2c.

Hint: $24 = 6(i_1 - 2) + i_1 R_2$

(d) Find the current i_2 and the voltage v_2 shown in Figure P 3.6-2b. Because of the equivalence, the current i_2 and the voltage v_2 shown in Figure P 3.6-2a are equal to the current i_2 and the voltage v_2 shown in Figure P 3.6-2b.

Hint: Use current division to calculate i_2 from i_1 .

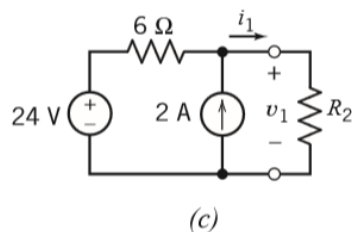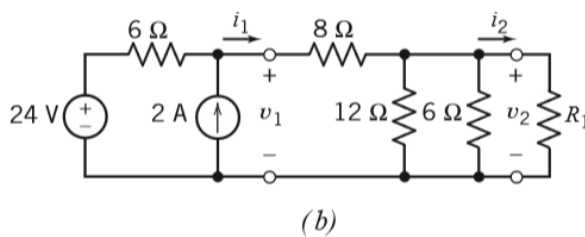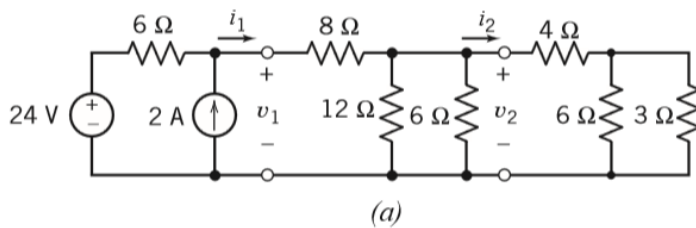(e) Determine the power absorbed by the 3-V resistance shown at the right of Figure P 3.6-2a.



13-2. (a) Determine values of R_1 and R_2 in Figure P3.6-4b that make the circuit in Figure P 3.6-4b equivalent to the circuit in Figure P 3.6-4a.

(b) Analyze the circuit in Figure P 3.6-4b to determine the values of the currents i_a and i_b .

(c) Because the circuits are equivalent, the currents i_a and i_b shown in Figure P 3.6-4b are equal to the currents i_a and i_b shown in Figure P 3.6-4a. Use this fact to determine values of the voltage v_1 and current i_2 shown in Figure P 3.6-4a.

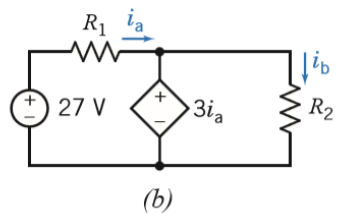
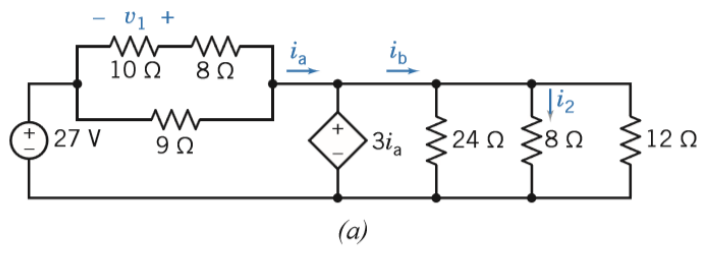


Figure P 3.6-4